

Day6-4X1_Multiplexer

#75daysRTL


A multiplexer is a data selector device that selects one input from several input lines, depending upon the enabled, select lines, and yields one single output.

A multiplexer of **2^n inputs has n select lines**, which are used to select which input line to send to the output. There is only one output in the multiplexer. We designed a 4x1 Multiplexer where for 4 input lines 1 output is selected.

Truth Table (Selection Lines)-

Select-S0	Select – S1	Output Line
0	0	A0
0	1	A1
1	0	A2
1	1	A3

Block Diagram –

 

Verilog Code –

```
module mux4_1(in,sel,out);
input [3:0]in;
input [1:0]sel;
output reg out;

always@(in,sel,out)
begin
case(sel)
```


```
2'b00:out=in[0];
2'b01:out=in[1];
2'b10:out=in[2];
2'b11:out=in[3];
endcase
```

TestBench Code-

```
module mux4_1_tb();
reg [3:0]in;
reg [1:0]sel;
wire out;

mux4_1 dut(in,sel,out);
initial begin
in=0;sel=0;
#10;
in=4'b1010;
sel=2'b01;
#10;
sel=2'b11;
#10;
sel=2'b00;
#10;
sel=2'b10;
#10;
$finish;
end
endmodule
```

Schematic View of 4X1 Multiplexerr-

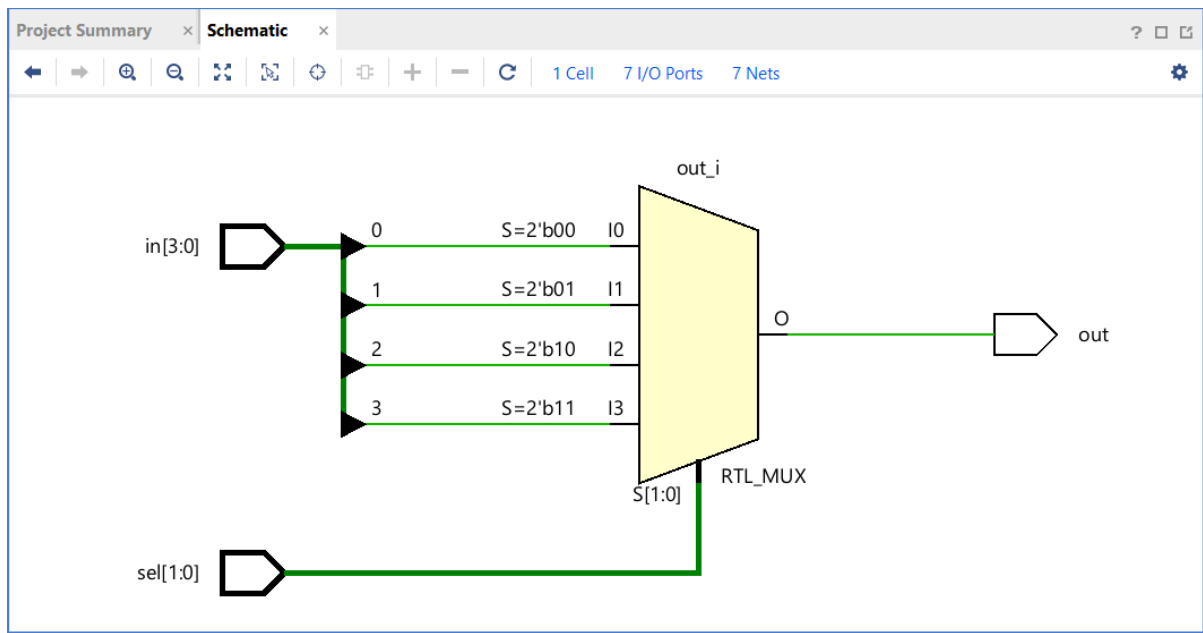

Simulation Result of 4X1 Multiplexer-

