

Day2-Full Adder using Half Adder

#75daysRTL

Full adder is a combinational circuit that consists of 3 inputs to generate a sum and carry it as output.

Generation of Full Adder-

1. Using Gates based on the Equation-

$$\text{Sum} = A \text{ xor } B \text{ xor } \text{Cin}$$

$$\text{Carry} = (A.B) + (B.\text{Cin}) + (A.\text{Cin})$$

To implement Full Adder using Gates we require **2XOR, 3AND, 2OR gates**.

2. Using Half Adder circuit- (Mostly Used)


Half adder is a combinational circuit in which a computer binary adds two binary inputs a & b to produce output sum & carry.

To implement Full Adder using Half Adder we require **2 Half Adders, 1OR gate**.

Truth Table-

Input A	Input B	Input Cin	Output Sum	Output Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Schematic View-

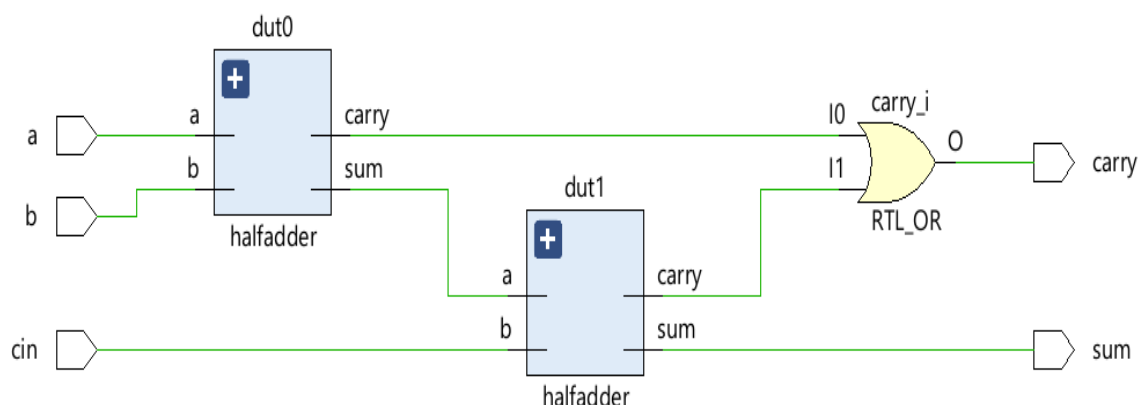

Verilog Code-

```
module fulladder(sum,carry,a,b,cin);
input a,b,cin;
output sum,carry;
wire sum1,sum2,carry1,carry2;
halfadder dut0(a,b,sum1,carry1);
halfadder dut1(sum1,cin,sum,carry2);
assign carry=carry1|carry2;
endmodule

module halfadder(a,b,sum,carry);
input a,b;
output sum,carry;
assign sum=a^b;
assign carry=a&b;
endmodule
```

TestBench Code-

```
module fulladder_tb( );
reg a,b,cin;
wire sum,carry;
fulladder uut(sum,carry,a,b,cin);
initial begin
a=0;b=0;cin=0;
#10 a=0;b=0;cin=1;
#10 a=0;b=1;cin=0;
#10 a=0;b=1;cin=1;
#10 a=1;b=1;cin=0;
#10 a=1;b=0;cin=0;
#10 a=0;b=1;cin=0;
#10 a=0;b=1;cin=1;
end
endmodule
```

Simulation Results-

